


Sequential Circuit Design: Part 1

- Design of memory elements
 - Static latches
 - Pseudo-static latches
 - Dynamic latches
- Timing parameters
- Two-phase clocking
- Clocked inverters

Krish Chakrabarty

1

Sequential Logic

 

2 storage mechanisms


- positive feedback
- charge-based

Krish Chakrabarty

2

Sequencing

 - *Combinational logic*
 - output depends on current inputs
- *Sequential logic*
 - output depends on current and previous inputs
 - Requires separating previous, current, future
 - Called *state* or *tokens*
 - Ex: FSM, pipeline



Krish Chakrabarty

3

Sequencing Cont.

- If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- Ex: fiber-optic cable
 - Light pulses (tokens) are sent down cable
 - Next pulse sent before first reaches end of cable
 - No need for hardware to separate pulses
 - But *dispersion* sets min time between pulses
- This is called *wave pipelining* in circuits
- In most circuits, dispersion is high
 - Delay fast tokens so they don't catch slow ones.

Krish Chakrabarty

4

Sequencing Overhead


- Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- Inevitably adds some delay to the slow tokens
- Makes circuit slower than just the logic delay
 - Called sequencing overhead
- Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence

Krish Chakrabarty

5

Sequencing Elements

 
- **Latch:** Level sensitive
 - a.k.a. transparent latch, D latch
- **Flip-flop:** edge triggered
 - A.k.a. master-slave flip-flop, D flip-flop, D register
- **Timing Diagrams**
 - Transparent
 - Opaque
 - Edge-trigger



Krish Chakrabarty

6


Flip-Flop: Timing Definitions

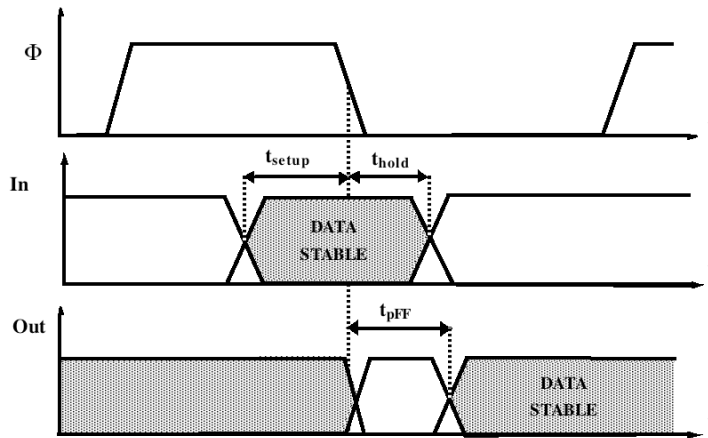

Krish Chakrabarty

7

Maximum Clock Frequency

 


$$t_{pFF} + t_{pcomb} + t_{setup} < T$$

Krish Chakrabarty

8

Latch Design

 - Pass Transistor Latch
- Pros
 - + Tiny
 - + Low clock load
- Cons
 - V_t drop
 - nonrestoring
 - backdriving
 - output noise sensitivity
 - dynamic
 - diffusion input




Used in 1970's

Krish Chakrabarty

9

Latch Design

 - Transmission gate
 - + No V_t drop
 - Requires inverted clock




Krish Chakrabarty

10

Latch Design

 - Inverting buffer
 - + Restoring
 - + No backdriving
 - + Fixes either
 - Output noise sensitivity
 - Or diffusion input
 - Inverted output




Krish Chakrabarty

11

Latch Design

 - Buffered input
 - + Fixes diffusion input
 - + Noninverting




Krish Chakrabarty

12

Latch Design

- Buffered output
+ No backdriving

 


- Widely used in standard cells
+ Very robust (most important)
- Rather large
- Rather slow (1.5 – 2 FO4 delays)
- High clock loading

Krish Chakrabarty

13

Latch Design

 - Tristate feedback
+ Static
– Backdriving risk




- Static latches are now essential

Krish Chakrabarty

14

Latch Design

 
- Datapath latch
 - + Smaller, faster
 - unbuffered input



Krish Chakrabarty

15

Design of Memory Elements

 


Positive edge-triggered D flip-flop


Why use inverters on outputs?

Skew Problem : $\bar{\Phi}$ may be delayed with respect to Φ (both may be 1 at the same time)

This is what happens-

 

Eliminating/Reducing skew:

 


Transmission gate acts a buffer, should have same delay as inverter

Krish Chakrabarty

16


Latch design

 

Krish Chakrabarty

17

Latch Design

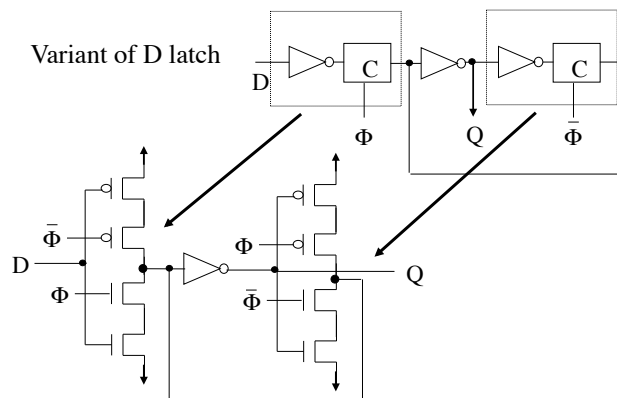


Krish Chakrabarty

18

Flip-Flop Design

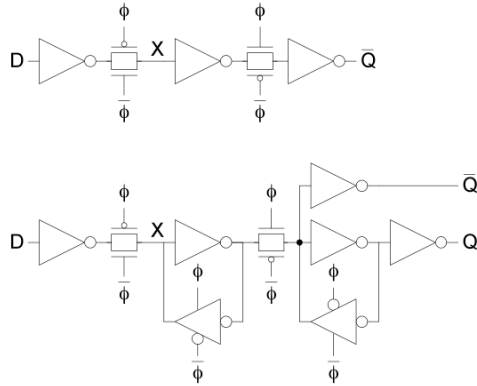- Flip-flop is built as pair of back-to-back latches




Krish Chakrabarty

19

Enable

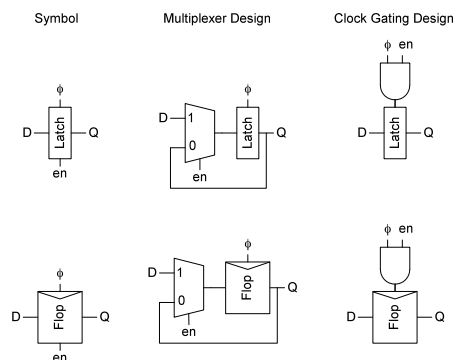- Enable: ignore clock when $en = 0$
 - Mux: increase latch D-Q delay
 - Clock Gating: increase en setup time, skew




Krish Chakrabarty

20

Reset

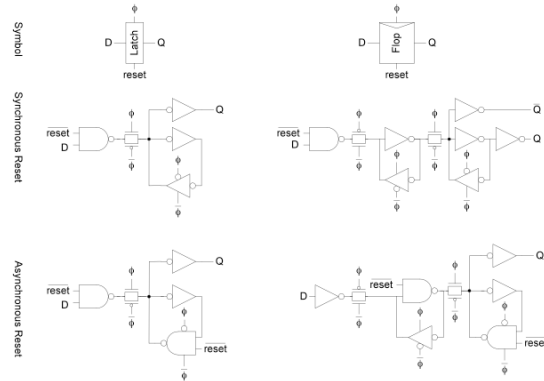- Force output low when reset asserted
- Synchronous vs. asynchronous




Krish Chakrabarty

21

Set / Reset

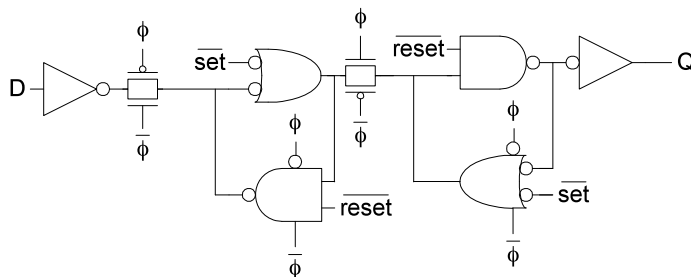- Set forces output high when enabled
- Flip-flop with asynchronous set and reset



Krish Chakrabarty

22


Dynamic Latches

- So far, all latches have been static-store state when clock is stopped but power is maintained
- Dynamic latches reduce transistor count
- Eliminate feedback inverter and transmission gate
- Latch value stored on the capacitance of the input (gate capacitance)

Krish Chakrabarty

23

Dynamic Latch and Flip-Flop


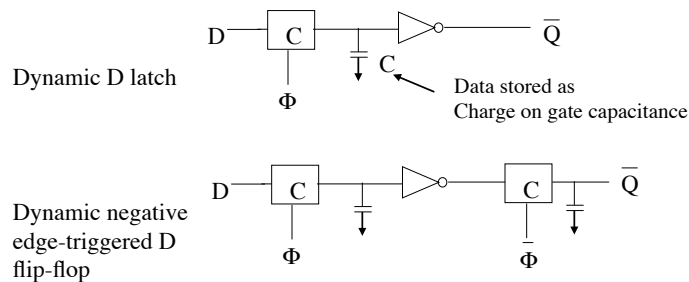


- Difficult to ensure reliable operation
- Similar to DRAM
- Refresh cycles are required

Krish Chakrabarty

24

Charge-Based Storage

  

Non-overlapping clocks



Schematic diagram

Pseudo-static Latch

Krish Chakrabarty

25

Master-Slave Flip-Flop

  

To reduce skew: generate complement of clock within the cell
Extra inverter per cell

Overlapping Clocks Can Cause

- Race Conditions
- Undefined Signals

Krish Chakrabarty

26


Two-Phase Clocking

- Inverting a single clock can lead to skew problems
- Employ two non-overlapping clocks for master and slave sections of a flip-flop
- Also, use two phases for alternating pipeline stages

Krish Chakrabarty

27


Two-Phase Clocking

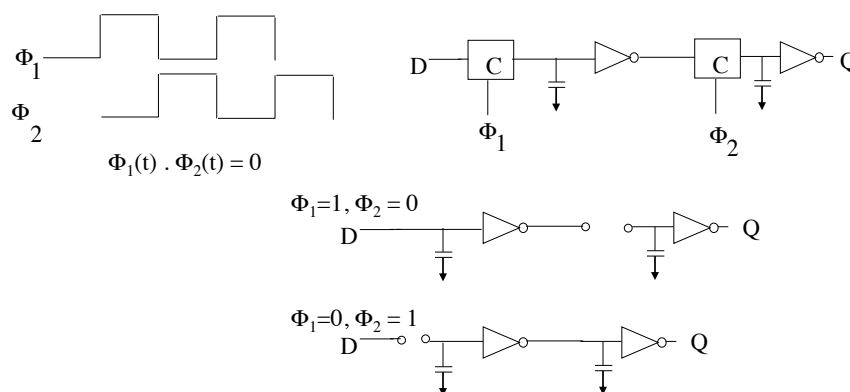

Krish Chakrabarty

28


2-phase non-overlapping clocks

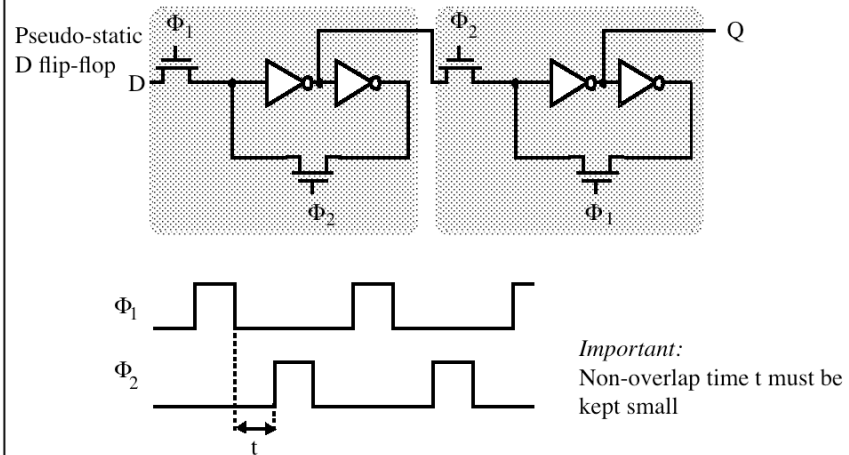

Krish Chakrabarty

29


2-phase dynamic flip-flop

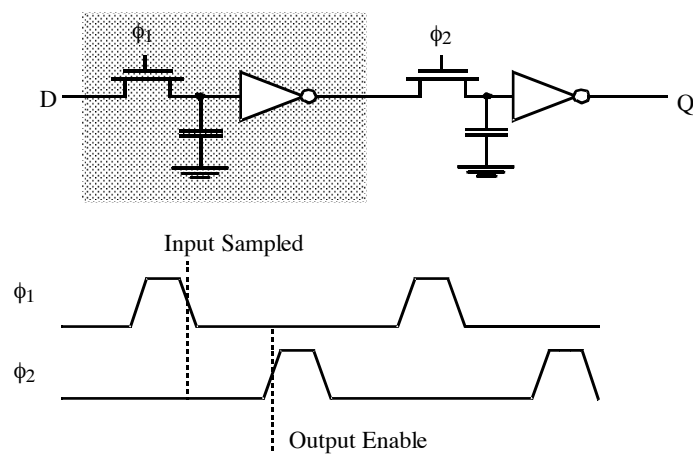

Krish Chakrabarty

30


Use of “p” Leakers

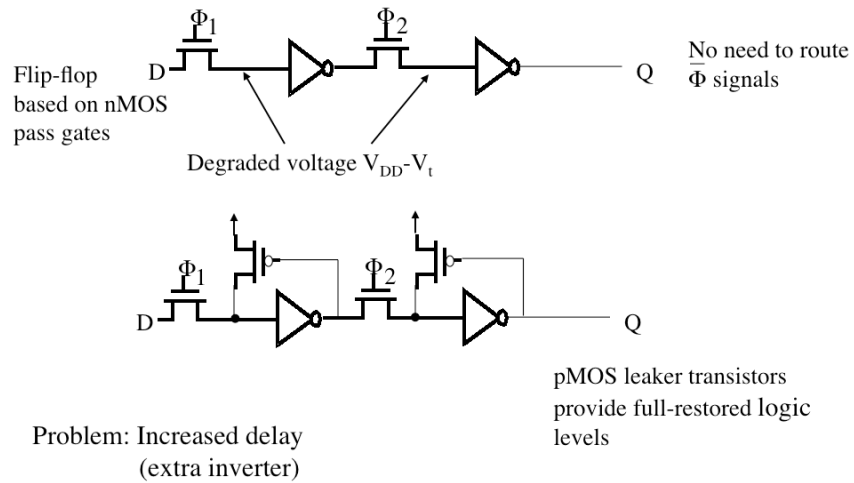

Krish Chakrabarty

31


Clocked Inverters

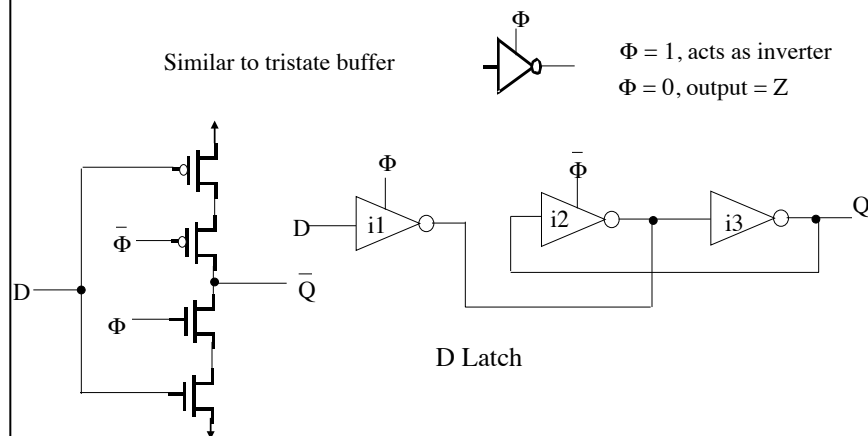

Krish Chakrabarty

32


Flip-flop insensitive to clock overlap

 

Krish Chakrabarty

33

C²MOS avoids Race Conditions

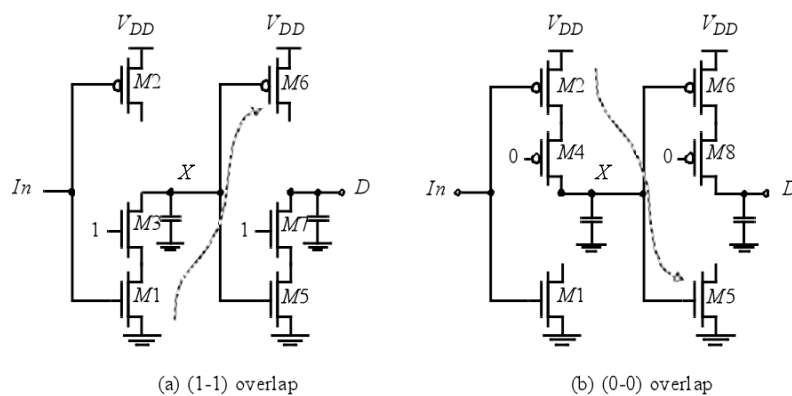

Krish Chakrabarty

34